

f. All of these capacitors didn't show the switch bouncing. This makes sense because all of these have a bigger capacitance than the one we used in class, which was small enough to prevent button bounces.

g.  $20\text{ k}\Omega$  is the worst case because it allows maximum current to flow. With maximum current flowing, the wires would have a lot of ~~energy~~ <sup>current</sup> which increases the chances of the button bouncing. With a  $50\text{ k}\Omega$  resistor, there is less current flowing in the circuit and the chances of electricity jumping between switch plates is less. Basically, the chances of button bouncing is reduced.

### Lab 3

1.a. The circuit would still work. If  $V_{in}$  goes down a little bit,  $V_{out}$  would start decreasing rapidly. Since the difference between  $V_+$  &  $V_-$  should be 0 and since  $V_{out}$ 's connection to  $V_+$ ,  $V_+$  would go down gradually and adjust itself so its equal to  $V_{in}$ . Soon  $V_{out}$  would start stop decreasing and stabilize. ~~so it's equal to  $V_+$  &  $V_-$ .~~



b.  $A = 10^4$

$V_{in} = 1V$

$V_{out} = V_+$

$V_{out} = (V_+ - V_-)A$

$V_{out} = (V_{out} - 1)A$

$V_{out} = V_{out}A - A$

$V_{out} - V_{out}A = -A$

$V_{out}(1-A) = -A$

$V_{out} = \frac{-A}{1-A} = \frac{-10^4}{1-10^4} \approx$

$V_{out} = \frac{10^4}{9999} \approx 1V$

2. a. From voltage divider circuit.

$V_{fb} = \frac{R_1}{R_1 + R_2} \times V_{out}$

b. We know  $V_{in} = V_{fb}$

$V_{out} = (V_{in} - V_{fb})A$   $V_{in} = \frac{R_1}{R_1 + R_2} \times A V_{out}$

$V_{out} = V_{in} \times \frac{R_1 + R_2}{R_1}$

$V_{out} = V_{in} \times \left[ 1 + \frac{R_2}{R_1} \right]$

c.  $A_v = \frac{V_{out}}{V_{in}} = \frac{V_{out}}{\frac{R_1}{R_1 + R_2} \times V_{out}} = \frac{R_1 + R_2}{R_1} = \left[ 1 + \frac{R_2}{R_1} \right] = \frac{V_{out}}{V_{in}}$



d.  $A_v = 11$   $A_v = 1 + \frac{R_2}{R_1}$

$R_1 = 10 \text{ k}\Omega$

$R_2 = ?$

$$11 = 1 + \frac{R_2}{10 \times 10^3}$$

$$11 = \frac{10 \times 10^3 + R_2}{10 \times 10^3}$$

$$11 \times 10 \times 10^3 = 10^4 + R_2$$

$$11 \times 10^4 - 10^4 = R_2$$

$$10^5 = R_2$$

$$R_2 = 100 \text{ k}\Omega$$

3. a.  $V_{\text{set}} = 2.5 \text{ V}$

if  $V_{\text{in}} = 0 \text{ V}$

$V_{\text{set}} = V_{\text{fb}}$

$$V_{\text{out}} = V_{\text{fb}} = \frac{V_{\text{in}} R_2}{R_1}$$

$$V_{\text{out}} = V_{\text{set}} = 2.5 \text{ V} \quad \text{since } \frac{R_2}{R_1} = 0.$$

if  $V_{\text{in}} = 5 \text{ V}$


$$V_{\text{out}} = \frac{5 R_2}{R_1} \text{ V}$$

b. The largest ratio would be  $3 R_2 / R_1$ , if  $V_{\text{in}} = 3 \text{ V}$ .

c. The largest ratio would be  $5 R_2 / R_1$ , if  $V_{\text{in}} = 5 \text{ V}$ .



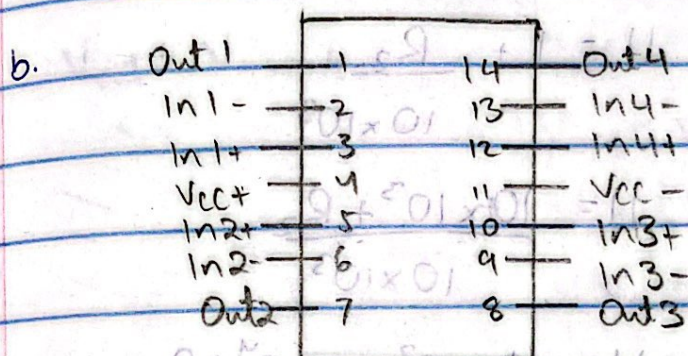4. a. There are 4 op amps in the TL974IN.



c. The maximum supply voltage is  $\pm 15$  V.

d. The minimum voltage is 2.7 V.

e. The power rails <sup>can</sup> provide voltages greater than 2.7 V, so we can operate this device.

f. The maximum  $V_{IO}$  is  $\pm 1$  V.

g.  $I_B$  typically is 200 - 750 nA. <sup>The</sup> device can produce currents upto 1000 nA too over the full range of operating temperatures.



## Design Challenge

3. a.  $V_{out} - V_{fb} = \frac{V_{fb} - V_{in}}{R_1} \times R_2$        $V_{set} = 2.5 \text{ V} = V_{fb}$   
 $R_2 = 30 \text{ k}\Omega$

a.  $V_{in} = 0$        $V_{out} = 2.5 \times \frac{30 \times 10^3}{50 \times 10^3} + 2.5$        $R_1 = 50 \text{ k}\Omega$

$$\left( \frac{30 \times 10^3}{50 \times 10^3} \right) = -4 \text{ V}$$

b.  $V_{in} = 5$        $V_{out} = \frac{(2.5 - 5)}{50 \times 10^3} \times 30 \times 10^3 + 2.5$

$$V_{out} = \underline{1}$$

$$V_{set} = V_{fb} = 2 \text{ V}$$

d.  $V_{in} = 5$        $V_{out} = \frac{(2 - 5)}{50 \times 10^3} \times 30 \times 10^3 + 2$

$$V_{out} = \underline{0.2 \text{ V}}$$

c.  $V_{in} = 0$        $V_{out} = \frac{2 - 0}{50 \times 10^3} \times 30 \times 10^3 + 2$

$$V_{out} = \underline{3.2 \text{ V}}$$

e.  $V_{dd}$  is 5 V.

f.  $V_{out} = 4 \text{ V}$        $V_{in} = 0$

$V_{out} = 1 \text{ V}$        $V_{in} = 5$

g. These values might differ if  $V_{set} \neq 2.5$ . The



makes the LED off time more pronounced.

4. As I press the button, I can see the length of the pulses increasing in the oscilloscope. As I turn the potentiometer, the intensity of the LED changes. This changes the range of voltage supplied to the LED. As a result, turning the LED potentiometer to the extreme ends turns off the LED. I can see this as  $V_{out}$ 's range rises in the oscilloscope. The light is blinking rapidly which makes it not pleasing.

5. When I attached the capacitors, the light stopped flickering. The quality of the blinks improved and we can see capacitor charging when before blinks. Like the previous problem, changing the potentiometer changed the intensity of the LED.